



California Polytechnic State University Pomona

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING

Digital Logic LAB
ECE 2300L

Lab#9

Prepared by

Paul Yang
Ryan Balatbat
Jason Nguyen

Presented to

Keji Baril

Introduction

Today we will try to use flip flop to create a sequential circuit

Objective

Using T-flip flops we will create a sequential counter that will go through the following numbers in the given order:

0,1,2,4,5,6,7


After 7 the counter will go back to 0 and repeat this sequence

Requirement

Given no input other than a clock input the circuit must cycle through the sequential sequence

State table T-flip flop

T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

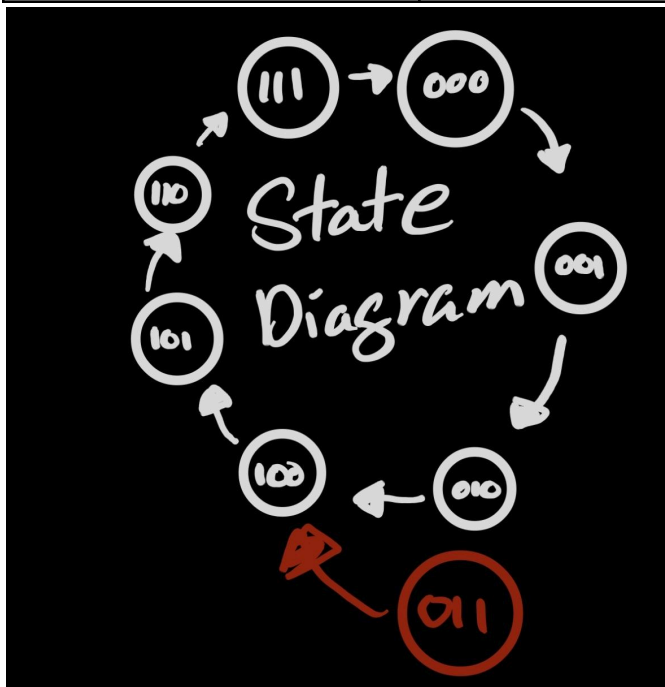

Start			Next			T(input)		
C2	C1	C0	C2	C1	C0	C2	C1	C0
0	0	0	0	0	1	0	0	1

0	0	1	0	1	0	0	1	1
0	1	0	1	0	0	1	1	0
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Parts List

1. Resistors
2. 7 segment display (common anode)
3. 74ls47
4. And gates
5. Or gates
6. Breadboard
7. Jumpers
8. Power Source
9. T flip flop (in this case we will make a t flip flop out of a j-k flip flop)

Design and Implementation

Not self-correcting

$$T_{C_2}$$

$C_2 \backslash C_1 C_0$	00	01	11	10
0	0	0	\bar{X}	$\bar{1}$
1	0	0	1	0

$$T_{C_2} = C_1 C_0 + \bar{C}_2 C_1$$

$$T_{C_1}$$


$C_2 \backslash C_1 C_0$	00	01	11	10
0	0	1	\bar{X}	1
1	0	1	1	0

$$T_{C_1} = C_0 + \bar{C}_2 C_1$$

$$T_{C_0}$$

$C_2 \backslash C_1 C_0$	00	01	11	10
0	1	1	\bar{X}	0
1	1	1	1	1

$$T_{C_0} = \bar{C}_1 + C_2$$

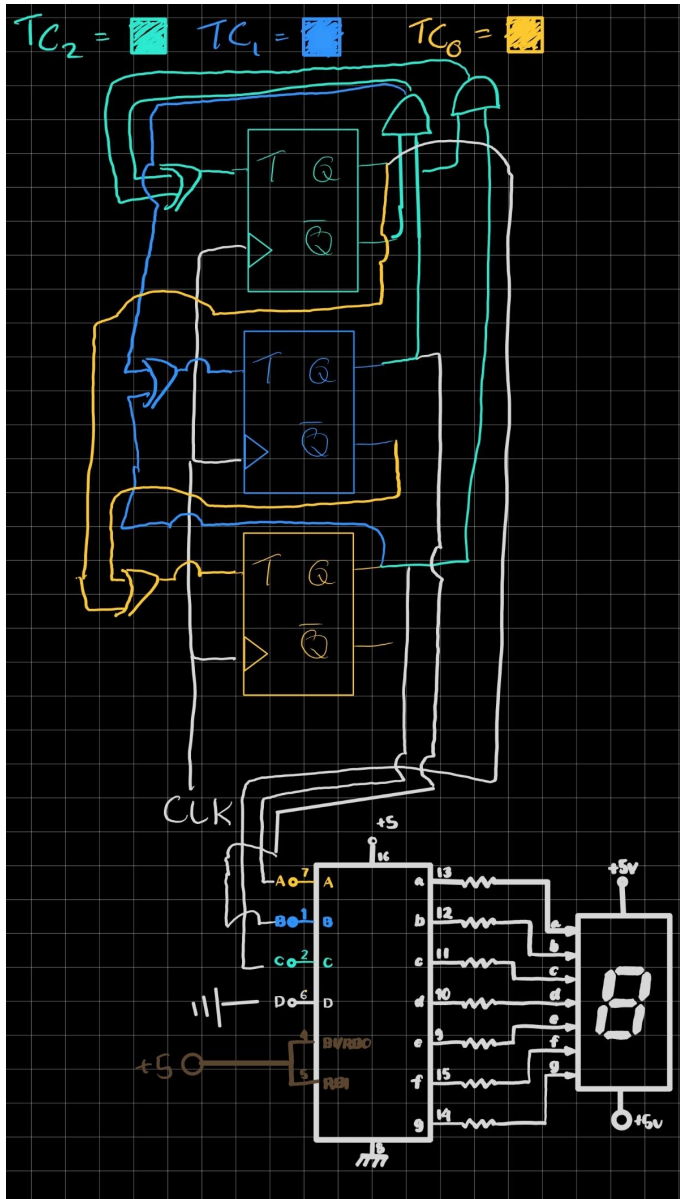

Self-Correcting given a 3 input

The difference between self-correcting and non-self-correcting is that in our nonself correcting we use our 3 as an I dont care since we assume it will never occur. However in order to make it self-correcting in the instance it is given a 3 input we just need to replace the dont care values with 1's in our K map. In this case, it will not effect a lot except out last flip-flop input as will be shown in the circuit diagram and is denoted in red.

$$T_{C_2}$$

$C_2 \backslash C_1 C_0$	00	01	11	10
0	0	0	1	1
1	0	0	1	0

$$T_{C_2} = C_1 C_0 + \overline{C_2} C_1$$

$$T_{C_1}$$


$C_2 \backslash C_1 C_0$	00	01	11	10
0	0	1	1	1
1	0	1	1	0

$$T_{C_1} = C_0 + \overline{C_2} C_1$$


$$T_{C_0}$$

$C_2 \backslash C_1 C_0$	00	01	11	10
0	1	1	1	0
1	1	1	1	1

$$T_{C_0} = \overline{C_1} + C_2 + C_0$$

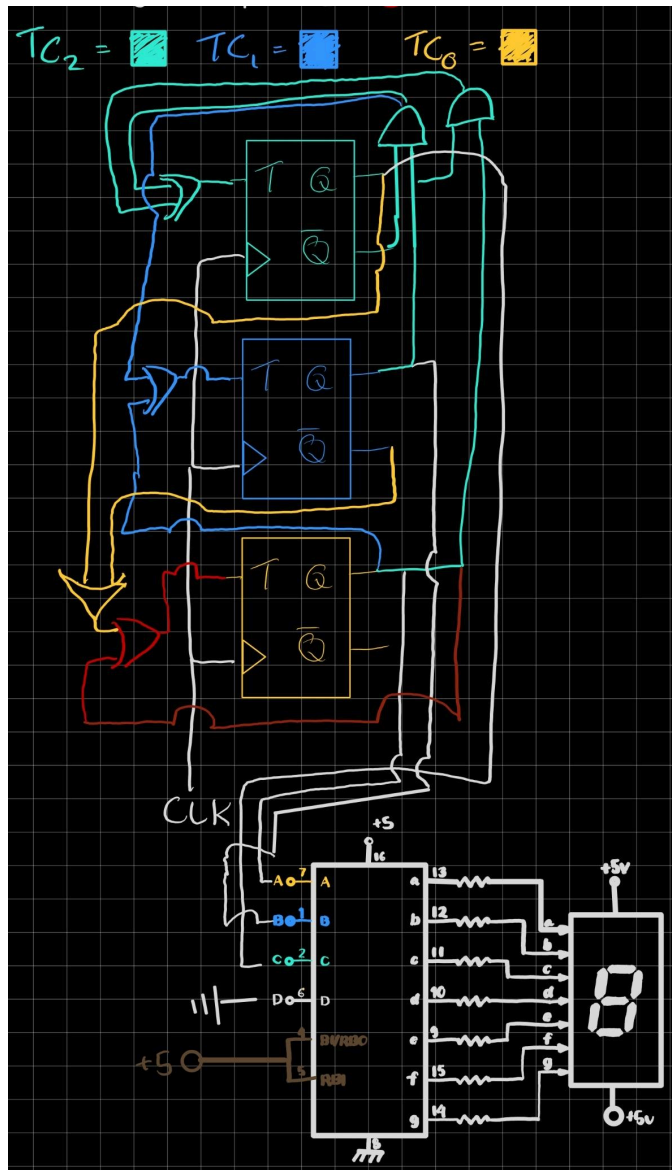

Test and set up

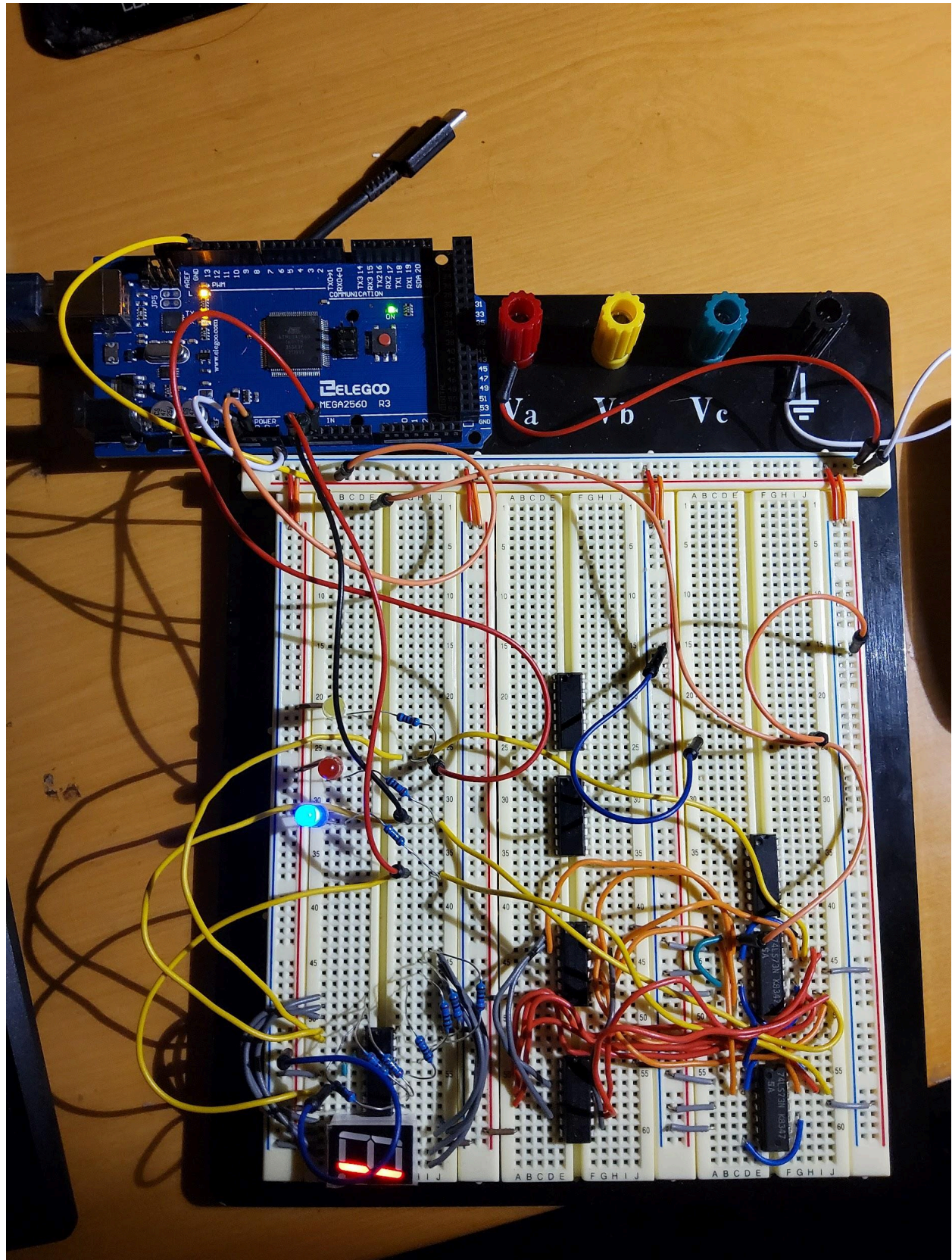

Results and Verification

These are the results of the given display recorded by an Arduino which is also acting as our clock input

```
Binary: 1 1 1 Decimal: 7
Binary: 0 0 0 Decimal: 0
Binary: 0 0 1 Decimal: 1
Binary: 0 1 0 Decimal: 2
Binary: 1 0 0 Decimal: 4
Binary: 1 0 1 Decimal: 5
Binary: 1 1 0 Decimal: 6
Binary: 1 1 1 Decimal: 7
Binary: 0 0 0 Decimal: 0
Binary: 0 0 1 Decimal: 1
Binary: 0 1 0 Decimal: 2
Binary: 1 0 0 Decimal: 4
Binary: 1 0 1 Decimal: 5
Binary: 1 1 0 Decimal: 6
Binary: 1 1 1 Decimal: 7
Binary: 0 0 0 Decimal: 0
Binary: 0 0 1 Decimal: 1
Binary: 0 1 0 Decimal: 2
Binary: 1 0 0 Decimal: 4
Binary: 1 0 1 Decimal: 5
Binary: 1 1 0 Decimal: 6
Binary: 1 1 1 Decimal: 7
Binary: 0 0 0 Decimal: 0
Binary: 0 0 1 Decimal: 1
Binary: 0 1 0 Decimal: 2
Binary: 1 0 0 Decimal: 4
Binary: 1 0 1 Decimal: 5
Binary: 1 1 0 Decimal: 6
Binary: 1 1 1 Decimal: 7
Binary: 0 0 0 Decimal: 0
Binary: 0 0 1 Decimal: 1
Binary: 0 1 0 Decimal: 2
```

CLR	T input	Present state	Next state
-----	---------	---------------	------------

H	C2	C1	C0	C2	C1	C0	C2	C1	C0
H	0	0	1	0	0	0	0	0	1
H	0	1	1	0	0	1	0	1	0
H	1	1	0	0	1	0	1	0	0
H	1	1	1	0	1	1	1	0	0
H	0	0	1	1	0	0	1	0	1
H	0	1	1	1	0	1	1	1	0
H	0	0	1	1	1	0	1	1	1
H	1	1	1	1	1	1	0	0	0

Arduino Code

```

int outPort=13;
int lsb=A0;
int nsb=A1;
int msb=A2;
void setup() {
    // put your setup code here, to run once:
    Serial.begin(9600);
    pinMode(outPort,OUTPUT);
    pinMode(lsb, INPUT);
    pinMode(nsb, INPUT);
    pinMode(msb, INPUT);
}

void loop() {
    // put your main code here, to run repeatedly:
    digitalWrite(outPort,HIGH);
    delay(500);
    digitalWrite(outPort,LOW);
    delay(500);
    int C2=analogRead(msb);
    int C5=1;
    if(C2<200){
        C5=0;
    }
    int C1=analogRead(nsb);
    int C4=1;

```

```


if (C1<200) {
    C4=0;
}
int C0=analogRead(1sb);
int C3=1;
if (C0<200) {
    C3=0;
}
int decimal=0;
if (C5==1) {
    decimal=decimal+4;
}
if (C4==1) {
    decimal=decimal+2;
}
if (C3==1) {
    decimal=decimal+1;
}
Serial.print("Binary: ");
Serial.print(C5);
Serial.print(' ');
Serial.print(C4);
Serial.print(' ');
Serial.print(C3);
Serial.print(' ');
Serial.print("Decimal: ");
Serial.print(decimal);
Serial.println(' ');
}

```

Post-Lab Questions

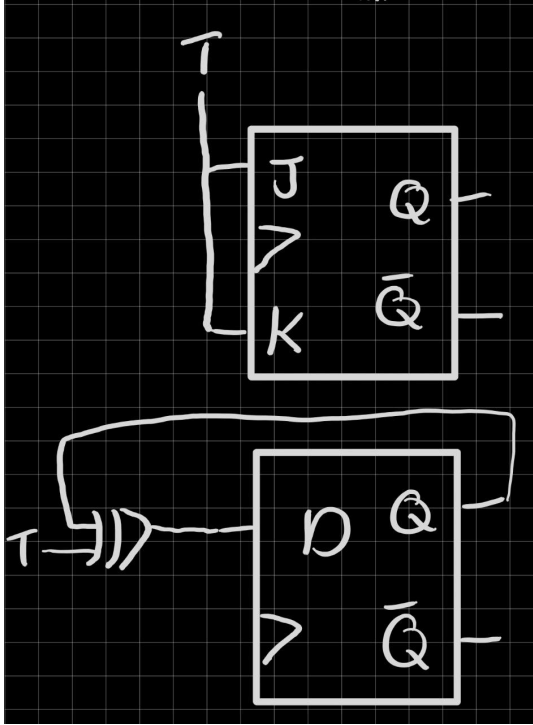1. **Is T- flip-flop commercially available? If so, draw the pin assignments from the Internet. If not, draw block diagrams for obtaining T- flip flops in two different ways**

T-flip flops are not commercially available. They however can be made from jk or d flip flops if wired a certain way



2. How many flip flops are needed to design a counter to count in the following sequence:

12, 20, 1, 0, and then repeat?

This sequence needs 5 flip flops because each flip flop essentially represents 1 bit thus to accommodate for a number as large as 20 (the largest number in the sequence) we would need 5 flip flops